

## INSTALLING A FLOATING-POINT COPROCESSOR INTO ATARI MEGA ST COMPUTER

(revised)

This text describes how to install a 68881 floating point processor into an Atari MEGA ST. The only other document on the subject that I could find was Keith Sabine's description (ref.1) of a circuit using two 74HC133 ICs and a 74HC32 to decode the address, the output of the 74HC32 being connected to the -AS input of the MC68881. That circuit is incomplete and contains an error (no "chip select" signal) such that IT CAN'T WORK, though it won't do any damage either. So here is a description of a correct way to connect the FPU. The Atari ST is an almost extinct computer breed, but as the 68881 is cheap these days, maybe somebody will find it worth the trouble to make this modification; total cost should not exceed 40 DEM.

---

### DISCLAIMER

Although this modification worked fine for me, it may not do so for you. I shall NOT be responsible for any damage, resulting from trying this modification, to your computer and other equipment, or any damage to anybody's life and health, or any galactic imbalance whatsoever. Whatever you do, you do at your own risk. Be advised that in an open computer there are exposed parts that are at mains line voltage (i.e. 220V AC) and you can easily get KILLED if you are not careful!

---

### Connecting the MC68881 to the MC68000:

---

NOTE: prefix "-" will be used for signals that are active in logical low state, e.g. -AS, -CS, etc.

According to ref.2 the MC68881 FPU connects to the MC68000 CPU not as a coprocessor, but rather as a "memory-mapped peripheral processor". Address decoding is system dependent; on the Atari the FPU addresses start at \$FFFA40. This address is decoded from A5 through A23, FC0 and FC1 in the user data space (FC2 is not used). Address signals A1 through A4 are not decoded but connected directly to the FPU. Output of the decoder circuit is connected to the active-low -CS (chip select) input of the FPU.

A0 input of the FPU is connected to logical 0 and -SIZE to +Vcc to indicate to the FPU that a 16-bit data bus is used.

The 16 least-significant data pins (D0-D15) are connected to the equivalent pins of the CPU. The 16 most significant data pins (D16-D31) are each connected to the corresponding less-significant pin (e.g. D0 is connected to D16, D1 to D17 ... D15 to D31).

-AS, -RESET, R/-W outputs of the CPU connect directly to the corresponding inputs of the FPU.

-DSACK1 output of the FPU connects to the -DTACK of the CPU; -DSACK0 is not used.

-LDS and -UDS from the CPU are gated together so that either can assert the active-low -DS input of the FPU.

-SENSE input of the FPU may optionally be connected to ground, but this is not required for correct operation. This signal is internally connected to ground and can be used to indicate to the external hardware that a FPU is present.

NC pin is reserved for Motorola use and not connected.

### Implementation:

---

I used the 12MHz FPU in a 68-pin PGA package, as I accidentally bought it very cheap. Two 74HC11s, one 74HC27 and one 74HC30 IC are used for address decoding, as shown in CIRCUIT.IMG. I so no point in designing a PCB for a project that I was not sure will function properly first time, and so the circuit was assembled on a piece of universal printed circuit board with 0.1inch raster (one-sided). All components were arranged approximately as shown in figure in LAYOUT.IMG, the interesting bit being that it was convenient to install this daughterboard upside-down, i.e. with chips below the board and all the connections (done with wire-wrap wires) on the upper

side. The reason for this was that the whole assembly occupied very little height in the computer housing, as the FPU fitted nicely between the MMU and the 32MHz clock. A connector with long pins was used, the pins protruding for about 12mm through the board, so that effectively the expansion port remained accesible for any other add-on that could fit above the FPU board. As the expansion port did not contain the +5V pins, a couple of pin sockets was soldered on the main board to the conveniently positioned strip supplying the Vcc to the MMU. Two long pins were soldered on the FPU board to mate with these sockets. Therefore the whole FPU board could be simply plugged-in or removed. This arrangement, however, proved unreliable and a piece of cable was added with a connector to mate to the spare power supply connector on MEGA's board.

A square opening was made in the FPU board, in the space below the FPU, to improve somewhat air circulation (the upside-down position is not exactly the optimum for cooling) and to facilitate the extraction of the FPU from its socket, if needed.

At first, I used the 8MHz clock signal taken from the expansion port, but later I added an integrated 12MHz clock to the board. As the FPU and CPU operate asynchronously, the FPU can work at any convenient clock frequency within its design limits, e.g. 8MHz to 12.5MHz for the 12MHz FPU. For a 16MHz FPU it might be convenient to take the clock signal from the nearby SHIFTER chip.

A switch Sw, mounted on the back side of the computer, was used to disable or enable the FPU (disable in "off" state), but after the initial testing this switch proved completely unnecessary as the FPU made no problems at all. So both the switch and the resistor can be omitted and the input to the NOR gate connected to logical 0. It is safe to turn the switch on/off during computer operation, but some applications may hang if the FPU is disabled during their execution.

Capacitors C1 (220 microF) and C2 (4.7microF, tantal) and C3-C5 (200nF), located near the Vcc pins of the chips, were used for decoupling.

The MC68881 dissipates about 0.75W in normal operation, so the whole board needs about 200mA at 5V supply; make sure that the power supply of your computer is adegate for the additional load, having in mind other installed devices such as a hard disk, etc. Maximum ambient temperature for the operation of the FPU is 70 degrees Centigrade, so ensure that the cooling is adequate.

Pin layouts:

-----  
See also PINS.IMG

MC68000 CPU (68pin DIP):

1=D4	17=-HALT	33= A5	49= Vcc (+5V)
2=D3	18=-RESET	34= A6	50= A21
3=D2	19=-VMA	35= A7	51= A22
4=D1	20= E	36= A8	52= A23
5=D0	21=-VPA	37= A9	53= GND
6=-AS	22=-BERR	38= A10	54= D15
7=-UDS	23=-IPL2	39= A11	55= D14
8=-LDS	24=-IPL1	40= A12	56= D13
9=R/-W	25=-IPL0	41= A13	57= D12
10=-DTACK	26= FC2	42= A14	58= D11
11=-BG	27= FC1	43= A15	59= D10
12=-BGACK	28= FC0	44= A16	60= D9
13=-BR	29= A1	45= A17	61= D8
14=Vcc (+5V)	30= A2	46= A18	62= D7
15=CLK	31= A3	47= A19	63= D6
16=GND	32= A4	48= A20	64= D5

MEGA-ST internal expansion port (2 x 32 pins):

b1=D4	b17=-HALT	a1= D5	a17= A20
b2=D3	b18=-RESET	a2= D6	a18= A19
b3=D2	b19=-VMA	a3= D7	a19= A18
b4=D1	b20= E	a4= D8	a20= A17
b5=D0	b21=-VPA	a5= D9	a21= A16
b6=-AS	b22=-BERR	a6= D10	a22= A15
b7=-UDS	b23=-IPL2	a7= D11	a23= A14

b8=-LDS	b24=-IPL1	a8= D12	a24= A13
b9=R/-W	b25=-IPL0	a9= D13	a25= A12
b10=-DTACK	b26= FC2	a10= D14	a26= A11
b11=-BG	b27= FC1	a11= D15	a27= A10
b12=-BGACK	b28= FC0	a12= GND	a28= A9
b13=-BR	b29= A1	a13= A23	a29= A8
b14=Vcc	b30= A2	a14= A22	a30= A7
b15=CLK	b31= A3	a15= A21	a31= A6
b16=GND	b32= A4	a16= Vcc	a32= A5

NOTE: pin layouts for the MC68000 and the expansion port are almost identical, except that the pins connected to the Vcc on the MC68000 are connected to GND on the expansion port.

12MHz Clock:

1= NC  
7= GND  
8= CLK  
14= Vcc (+5V)

MC68881 FPU (68pin PGA):

K  A1	R/-W	GND*	-DSACK1	D30	D29	D27	D26	D24	D22
J  A3	Vcc**	-CS	-DSACK0	D31	D28	D25	GND	D23	D21
H  -AS	A2	A0					Vcc	GND**	D19
G  -DS	A4							D20	D18
F  -SIZE	GND**							D17	D16
E  NC	Vcc							Vcc	GND
D  -RESET	GND**							D12	D15
C  GND	CLK	GND					D9	D13	D14
B  Vcc*	GND*	GND*	-SENSE	D2	D5	GND	Vcc	D10	D11
A  Vcc**	GND*	D0	D1	D3	D4	D6	D7	D8	GND**

1 2 3 4 5 6 7 8 9 10

The following is copied from ref.2, whatever it means:

\* = new assignment for the A93N mask  
\*\*= reserved for future Motorola use

Pin group	Vcc	GND
D31-D16	H8	J8
D15-D00	B8	B7
-DSACK1, -DSACK0, int.logic	E2, E9	A2, B2, B3, B4, C3, E10, K3
Separate	--	C1
Extra	A1, B1, J2	A10, D2, F2, H9

I just connected all the \* and \*\* pins and it worked fine.

Performance:

-----  
The increase in floating-point performance relative to the unmodified computer was impressive. GEMBENCH reported an improvement of about 1200% with the 8MHz FPU clock and about 1400% with the 12MHz clock. Rotation of a simple 3D view in DynaCadd 2.0 was speeded up by more than 500%, taking less than 5 seconds instead of original 25 seconds. Whetstone benchmark in Prospero FORTRAN reported values of about 175 (at 8MHz) and 200 (at 12MHz) relative to 50 "kwhets" without the FPU. The interesting thing to note was that there was not a significant gain in performance when the FPU clock frequency was changed from 8MHz to 12MHz. Obviously, in most applications the non-floating-point operations take a lot of CPU time. A conclusion might be made that, unless the user runs mostly applications that are VERY "floating-point intensive" there is not much point in installing a very fast FPU, except if one is accidentally available. The lower-performance 8MHz chip would do almost the same job.

NOTE 1: Documentation for GEMBENCH stated that some FPU boards "hang when bombarded with data...". That problem did not appear with this board when the 8MHz clock was used. It DID appear, however, and only in GEMBENCH (all other programs worked fine), with 12MHz clock, but ONLY when I used a gate from a 74HC08 to buffer the clock. When the clock signal was fed directly to the FPU everything was back to normal (the 74HC08 was then removed as

unnecessary). I did not have an oscilloscope to confirm it, but perhaps the problem could be attributed to inadequate capacitive decoupling that could not cope with continuous switching transients in the additional chip. This behaviour was experienced while the 200nF decoupling capacitors were not installed, but the test was not repeated after they were added.

NOTE 2: Some applications may not recognize the presence of a FPU unless the \_FPU cookie is installed (TOS 2.06 + SYSINFO reported a "SFP004 or compatible" FPU, with cookie value set to \$00010000).

#### Revision

-----

This document has been revised to correct several minor discrepancies between the original text and the actually built circuit, relating to the power supply cable and the decoupling capacitors. Also, some typing errors in the text have been corrected and my e-mail address updated.

#### References:

-----

1. Keith Sabine: 68881 for the 1040, June 19th 1991
2. Motorola semiconductor technical data: M68000 Family Reference;

Beograd, October 1996

Djordje Vukovic  
e-mail: vdjole@EUnet.yu  
or: vdjole@sezam.co.yu (unreliable)

-----\*-----